

## Project #1\buck.m

```
1 % ID Number: 229,506
2 % ECE 31033 - Project #1
3 % buck.m
4
5 % The file (buck.m) contains the Forward Euler integration algorithm within a while
6 % loop (FOR LOOPS ARE NOT ALLOWED). buck is not a function. The file buck.m only
7 % contains a single while loop (i.e. while (t(k)<tend)) to solve for all circuit voltages
8 % and currents of your buck converter. Within the while loop, you will call the
9 % function sw at each time instant to determine the value of your transistor gate
10 % (on or off). Voltages of currents and voltages of circuit components must be
11 % determined within the while loop.
12 while t_vec(k) < tend
13     if (ideal_boolean) % If the circuit is ideal.
14         switch_state(k) = sw(D, t_vec(k)); % calling sw.m
15
16         % Inductor Current and Load Voltage Calculation
17         i_L_vec(k+1) = i_L_vec(k) + dt * ((switch_state(k)) * V_in - V_load_vec(k)) / L;
18         V_load_vec(k+1) = V_load_vec(k) + dt * ((i_L_vec(k) - (V_load_vec(k) / R_load)) / C);
19
20         % Switch 1 and 2: Voltage and Current Calculations
21         if(switch_state(k))
22             V_switch1(k+1) = V_in;
23             i_switch1(k+1) = i_L_vec(k+1) * switch_state(k);
24
25             V_switch2(k+1) = 0;
26             i_switch2(k+1) = 0;
27
28             V_L_vec(k+1) = V_in - V_load_avg;
29         else
30             V_switch1(k+1) = 0;
31             i_switch1(k+1) = 0;
32
33             V_switch2(k+1) = -1 * V_in;
34             i_switch2(k+1) = i_L_vec(k) * (1 - switch_state(k));
35
36             V_L_vec(k+1) = -1 * V_load_avg;
37         end
38
39         % Capacitor: Voltage and Current Calculations
40         i_C_vec(k+1) = i_L_vec(k) - (V_load_vec(k) / R_load);
41         V_C_vec(k+1) = V_load_vec(k+1);
42
43         % Load: Current Calculation
44         i_load_vec(k+1) = V_load_vec(k+1) / R_load;
45
46     else % If the circuit is non ideal.
47         switch_state(k) = sw(D_non_ideal, t_vec(k)); % calling sw.m
48
49         if(switch_state(k))
50             %i_L_vec(k+1) = i_L_vec(k) + dt * ((V_in - V_T_on - V_load_vec(k) - (R_T_on *
i_L_vec(k)))) / L; %i_L
```

```

51     i_L_vec(k+1) = i_L_vec(k) + dt * ((V_in - V_T_on - V_load_vec(k) - (R_T_on *
i_L_vec(k))) / L);    %i_L
52
53     % Switch 1: Voltage and Current Calculations
54     V_switch1(k+1) = 0;
55     i_switch1(k+1) = i_L_vec(k+1);
56     P_switch1(k+1) = (R_T_on * i_L_vec(k+1) + V_T_on) * i_L_vec(k+1);
57
58     % Switch 2: Voltage and Current Calculations
59     V_switch2(k+1) = V_D_on + (R_D_on * i_L_vec(k+1)) - V_in;
60     i_switch2(k+1) = 0;
61     else
62     i_L_vec(k+1) = i_L_vec(k) + dt * ((-1 * V_load_vec(k) - V_D_on - (R_D_on *
i_L_vec(k))) / L);
63
64     % Switch 1: Voltage and Current Calculations
65     V_switch1(k+1) = V_in + (R_D_on * i_L_vec(k+1)) + V_D_on;
66     i_switch1(k+1) = 0;
67
68     % Switch 2: Voltage and Current Calculations
69     V_switch2(k+1) = 0;
70     i_switch2(k+1) = i_L_vec(k+1);
71     P_switch2(k+1) = (R_D_on * i_L_vec(k+1) + V_D_on) * i_L_vec(k+1);
72     end
73
74     V_load_vec(k+1) = V_load_vec(k) + dt * ((i_L_vec(k) - (V_load_vec(k) / R_load)) / C);
%V_load
75     end
76
77     % Increment the time and index
78     t_vec(k + 1) = t_vec(k) + dt;
79     k = k + 1;
80 end

```